

Liane Yanglian, net ID: xy48,
Feb.23, 2017,
CS 250

CS 250 Homework 3

1.

(a)

Truth Table
Formula: $\text{out} = !B * C + (A+B) * !C$

A	B	C	!B	!B*C	!C	A+B	(A+B)*!C	Out
0	0	0	1	0	1	0	0	0
0	0	1	1	1	0	0	0	1
0	1	0	0	0	1	1	1	1
0	1	1	0	0	0	1	0	0
1	0	0	1	0	1	1	1	1
1	0	1	1	1	0	1	0	1
1	1	0	0	0	1	1	1	1
1	1	1	0	0	0	1	0	0

(b) Please see circuit1.circ.

(c)

The sum-of-product Boolean functions for out1 and out2 are, respectively:

$\text{Out1} = (!A \& !B \& !C) \mid (!A \& B \& C) \mid (A \& !B \& C)$, or, alternatively expressed,
 $\text{Out1} = !A * !B * !C + !A * B * C + A * !B * C$

$\text{Out2} = (!A \& !B \& !C) \mid (!A \& !B \& C) \mid (!A \& B \& !C)$, or, alternatively expressed,
 $\text{Out2} = !A * !B * !C + !A * !B * C + !A * B * !C$

(d) Please see circuit2.circ.


2. Please see adder.circ.

3.

(a)

Here are the state transition diagrams for out 1 and out2, respectively.

State Transition Diagram for out 1

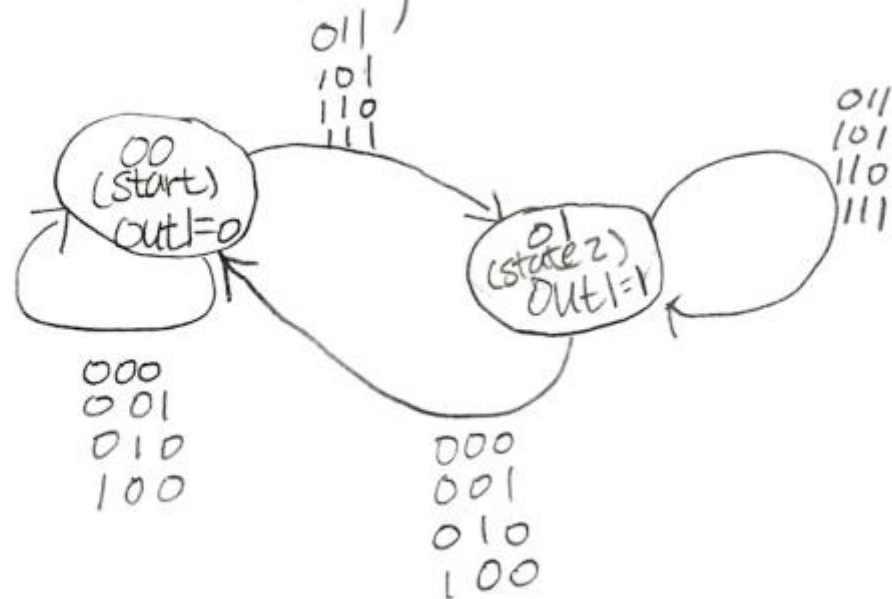

State Transition Diagram for out 2



(b)

Truth Table for Out1

(Since there are only two states for out1, I employed 1 D flip-flop, but I included both D0 and D1, and Q1 and Q0 here just in case.)

Current State (Q1)	Current State (Q0)	Output	In1	In2	In3	Next State (D0)	Next State (D1)
0	0 (start)	0 (closed)	0	0	0	0 (start)	0
0	0 (start)	0	0	0	1	0 (start)	0
0	0 (start)	0	0	1	0	0 (start)	0
0	0 (start)	0	0	1	1	1 (state2)	0
0	0 (start)	0	1	0	0	0 (start)	0
0	0 (start)	0	1	0	1	1 (state2)	0
0	0 (start)	0	1	1	0	1 (state2)	0
0	0(start)	0	1	1	1	1 (state2)	0
0	1 (state2)	1	0	0	0	0 (start)	0
0	1 (state2)	1	0	0	1	0 (start)	0
0	1 (state2)	1	0	1	0	0 (start)	0
0	1 (state2)	1	0	1	1	1 (state2)	0
0	1 (state2)	1	1	0	0	0 (start)	0
0	1 (state2)	1	1	0	1	1 (state2)	0
0	1 (state2)	1	1	1	0	1 (state2)	0
0	1 (state2)	1	1	1	1	1 (state2)	0

Truth Table for Out2

Current State (Q1)	Current State (Q2)	Output	In1	In2	In3	Next State (D1)	Next State (D0)
0(start)	0(start)	0(closed)	0	0	0	0	0
0	0	0	0	0	1	0	1
0	0	0	0	1	0	0	1
0	0	0	0	1	1	0	0
0	0	0	1	0	0	0	1
0	0	0	1	0	1	0	0
0	0	0	1	1	0	0	0
0	0	0	1	1	1	0	0
0	1	0	0	0	0	1	1
0	1	0	0	0	1	1	0
0	1	0	0	1	0	1	0
0	1	0	0	1	1	1	1
0	1	0	1	0	0	1	0
0	1	0	1	0	1	1	1
0	1	0	1	1	0	1	1
0	1	0	1	1	1	1	1
1	0	1	0	0	0	1	1
1	0	1	0	0	1	1	0
1	0	1	0	1	0	1	0
1	0	1	0	1	1	1	1
1	0	1	1	0	0	1	0
1	0	1	1	0	1	1	1
1	0	1	1	1	0	1	1
1	0	1	1	1	1	1	1
1	1	1	0	0	0	0	0
1	1	1	0	0	1	0	1
1	1	1	0	1	0	0	1
1	1	1	0	1	1	0	0
1	1	1	1	0	0	0	1
1	1	1	1	0	1	0	0
1	1	1	1	1	0	0	0
1	1	1	1	1	1	0	0

(c) Please see fsm.circ.

For out1, the sum-of-products formula I used is:

$(!Q0 \& in1 \& in2 \& in3) | (!Q0 \& in1 \& in2 \& !in3) | (!Q0 \& in1 \& !in2 \& in3) | (!Q0 \& !in1 \& in2 \& in3) | (Q0 \& in1 \& in2 \& in3) | (Q0 \& in1 \& in2 \& !in3) | (Q0 \& in1 \& !in2 \& in3) | (Q0 \& !in1 \& in2 \& in3)$

For out 2, the sum-of-products formula I used for D1 and D0 are respectively:

If common =

$(!Q1 \& Q0 \& !in1 \& !in2 \& !in3) | (!Q1 \& Q0 \& !in1 \& in2 \& in3) | (!Q1 \& Q0 \& in1 \& in2 \& !in3) | (!Q1 \& Q0 \& in1 \& in2 \& in3) | (!Q1 \& Q0 \& in1 \& !in2 \& in3) | (Q1 \& !Q0 \& !in1 \& !in2 \& !in3) | (Q1 \& !Q0 \& !in1 \& in2 \& in3) | (Q1 \& !Q0 \& in1 \& in2 \& !in3) | (Q1 \& !Q0 \& in1 \& in2 \& in3) | (Q1 \& !Q0 \& !in1 \& !in2 \& in3),$

This is the common part that I calculated separately and then computed with the rest of the formula for D1 and that for D0 respectively in order to get out2 in the end.

Then D1 =

$Common | (!Q1 \& Q0 \& in1 \& !in2 \& !in3) | (!Q1 \& Q0 \& !in1 \& !in2 \& in3) | (!Q1 \& Q0 \& !in1 \& in2 \& !in3) | (Q1 \& !Q0 \& in1 \& !in2 \& !in3) | (Q1 \& !Q0 \& !in1 \& !in2 \& in3) | (Q1 \& !Q0 \& !in1 \& in2 \& !in3).$

And D0 =

$Common | (!Q1 \& !Q0 \& in1 \& !in2 \& !in3) | (!Q1 \& !Q0 \& !in1 \& !in2 \& in3) | (!Q1 \& !Q0 \& !in1 \& in2 \& !in3) | (Q1 \& Q0 \& in1 \& !in2 \& !in3) | (Q1 \& Q0 \& !in1 \& !in2 \& in3) | (Q1 \& Q0 \& !in1 \& in2 \& !in3).$